

NOISE IN SC CIRCUITS

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca


Course Goals

- **Deepen Understanding of CMOS analog circuit design through a top-down study of a modern analog system**
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- **Develop circuit insight through brief peeks at some nifty little circuits**
The circuit world is filled with many little gems that every competent designer ought to recognize.

Date	Lecture			Ref	Homework
2008-01-07	RS 1	Introduction: MOD1 & MOD2	S&T 2-3, A	Matlab MOD2	
2008-01-14	RS 2	Example Design: Part 1	S&T 9.1, J&M 10	Switch-level sim	
2008-01-21	RS 3	Example Design: Part 2	J&M 14, S&T B	Q-level sim	
2008-01-28	TC 4	Pipeline and SAR ADCs	J&M 11,13	Pipeline DNL	
2008-02-04	ISSCC – No Lecture				
2008-02-11	RS 5	Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B	CTMOD2; Proj.	
2008-02-18	Reading Week – No Lecture				
2008-02-25	RS 6	Comparator and Flash ADC	J&M 7		
2008-03-03	TC 7	SC Circuits	Raz 12, J&M 10		
2008-03-10	TC 8	Amplifier Design			
2008-03-17	TC 9	Amplifier Design			
2008-03-24	TC 10	Noise in SC Circuits	S&T C		
2008-03-31	RS 11	Switching Regulator			
2008-04-07	Project Presentations				
2008-04-14	TC 12	Matching & MM-Shaping		Project Report	

NLCOTD: Gain Booster CMFB

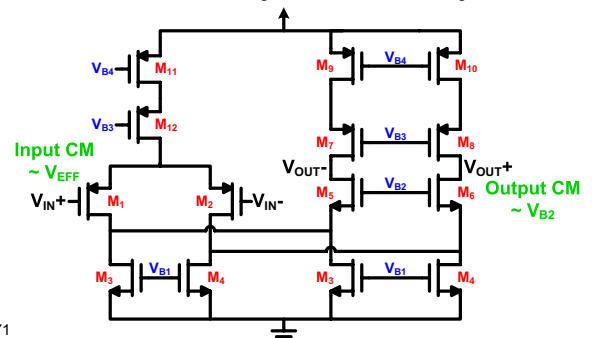- **Need CMFB for Gain Booster**
One option is to use standard CT CMFB (Lecture 9)
Is there an easier way with less circuitry?




Highlights

(i.e. What you will learn today)

 - 1. How to analyze noise in switched-capacitor circuits**
- 2. Significance of switch noise vs. OTA noise**
 - Power efficient solution
 - Impact of OTA architecture
- 3. Design example for $\Delta\Sigma$ modulator**


Review

- **Previous analysis of kT/C noise (ignoring OTA/opamp noise)**
 - Phase 1: kT/C_1 noise (on each side)
 - Phase 2: kT/C_1 added to previous noise (on each side)
 - Total Noise (input referred): $2kT/C_1$
 - Differentially: $4kT/C_1$



- **SNR**
 - Total noise power: $4kT/C_1$
 - Signal power: $V^2/2$
 - SNR: $V^2C_1/8kT$
- **SNR (single-ended)**
 - Total noise power: $2kT/C_1$ (sampling capacitor C_1)
 - Signal power: $V^2/2$ (signal from $-V$ to V)
 - SNR: $V^2C_1/4kT$

 
- **Single-Ended Example**
 Noise current from each transistor is $\overline{i_n^2} = 4kT\gamma g_m$
 Assume $\gamma = 2/3$



- Single-Ended Example
 - Thermal noise in single-ended OTA
 - Assuming paths match, tail current source M_5 does not contribute noise to output
 - PSD of noise voltage in M_1 (and M_2): $\frac{8kT}{3g_{m1}}$
 - PSD of noise voltage in M_3 (and M_4): $\frac{8kTg_{m3}}{3g_{m1}^2}$
 - Total input referred noise from $M_1 - M_4$

$$S_{n,eq} = \frac{16kT}{3g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right) = \frac{16kT}{3g_{m1}} n_f$$
 - Noise factor n_f depends on architecture

 - **Analyze output noise in single-stage OTA**
Use capacitive feedback in the amplification / integration phase of a switched-capacitor circuit



- **Transfer function of closed loop OTA**

$$H(s) = \frac{V_{OUT}}{V_{in,eq}} = \frac{G}{1 + s/\omega_o}$$

where the DC Gain and 1st-pole frequency are

$$G \approx \frac{1}{\beta} = 1 + C_1 / C_2 \quad \omega_o = \frac{\beta g_{m1}}{C_o}$$

Load capacitance C_O depends on the type of OTA – for a single-stage, it is $C_L + C_1 C_2 / (C_1 + C_2)$, while for a two-stage, it is the compensation capacitor C_C

- **Integrate total noise at output**


$$\begin{aligned}\overline{V_{OUT}^2} &= \int_0^\infty S_{n,eq}(f) |H(j2\pi f)|^2 df \\ &= \frac{16kT}{3g_{m1}} n_f \frac{\omega_o}{4} G^2 \\ &= \frac{4kT}{3\beta C_o} n_f\end{aligned}$$

Minimum output noise for $\beta=1$ is $\frac{4kT}{3C_o} n_f$

Not a function of g_{m1} since bandwidth is proportional to g_{m1} while PSD is inversely proportional to g_{m1}

OTA with capacitive feedback

- Graphically...

 

Noise is effectively filtered by the equivalent brick wall response with a cut-off frequency of $\pi f_o/2$
Total noise at V_{OUT} is the integral of the noise within the brick wall filter (area is simply $\pi f_o/2 \times 1/\beta^2$)


ECE1371

10-13

Sampled Thermal Noise

- What happens to noise once it gets sampled?


Total noise power is the same
Noise is aliased – folded back from higher frequencies to lower frequencies
PSD of the noise increases significantly

 

ECE1371

10-14

Sampled Thermal Noise

 

- Same total area, but PSD is larger from 0 to $f_s/2$

$$S_{vout}(f) = \frac{G^2 S_{n,eq}}{4\tau f_s/2} = \frac{\overline{V_{OUT}^2}}{f_s/2} = \frac{4kT}{3\beta C_o} n_f \frac{1}{f_s/2}$$

Low frequency PSD $G^2 S_{n,eq}$ is increased by $\frac{1}{2\tau f_s} = \frac{\pi f_{3dB}}{f_s}$

ECE1371

10-15

Sampled Thermal Noise

- $1/f_{3dB}$ is the settling time of the system, while $1/2f_s$ is the settling period for a two-phase clock

$$e^{-\frac{1/2f_s}{\tau}} < 2^{-(N+1)}$$

$$\frac{\pi f_{3dB}}{f_s} > (N+1)\ln 2$$

PSD is increased by at least $(N+1)\ln 2$

If $N = 10$ bits, PSD is increased by 7.6, or 8.8dB

- This is an inherent disadvantage of sampled-data compared to continuous-time systems


But noise is reduced by oversampling ratio after digital filtering

ECE1371

10-16

Noise in a SC Integrator

 - Using the parasitic-insensitive SC integrator



- Two phases to consider

1) Sampling Phase

Includes noise from both ϕ_1 switches

2) Integrating Phase


Includes noise from both ϕ_2 switches and OTA

ECE1371

10-17

Noise in a SC Integrator

- Phase 1: Sampling

 

Noise PSD from two switches: $S_{Ron}(f) = 8kTR_{ON}$

Time constant of R-C filter: $\tau = 2R_{ON}C_1$

PSD of noise voltage across C_1

$$S_{C1}(f) = \frac{8kTR_{ON}}{1 + (2\pi f\tau)^2}$$

ECE1371

10-18

Noise in a SC Integrator

- Phase 1: Sampling

Integrated across entire spectrum, total noise power in C_1 is

$$\overline{V_{C1,sw1}^2} = \frac{8kTR_{ON}}{4\tau} = \frac{kT}{C_1}$$

Independent of R_{ON} (PSD is proportional to R_{ON} , bandwidth is inversely proportional to R_{ON})


After sampling, charge is trapped in C_1

ECE1371

10-19

Noise in a SC Integrator

- Phase 2: Integrating

 

- Two noise sources - switches and OTA

Noise PSD from two switches: $S_{Ron}(f) = 8kTR_{ON}$


Noise PSD from OTA: $S_{vn,eq}(f) = \frac{16kT}{3g_{m1}} n_f$

Noise voltage across C_1 charges to $\sqrt{2}V_{Ron} - V_{n,eq}$

10-20

Noise in a SC Integrator

- What is the time-constant?

 

Analysis shows that $Z_{IN} = \frac{1/sC_2 + R_L}{1 + g_{m1}R_L}$

For large R_L , assume that $Z_{IN} = \frac{1}{g_{m1}}$

Resulting time constant $\tau = (2R_{ON} + 1/g_{m1})C_1$

ECE1371

10-21

Noise in a SC Integrator

- Total noise power with both switches and OTA on integrating phase

$$\begin{aligned} \overline{V_{C1,op}^2} &= \frac{S_{vn,eq}(f)}{4\tau} \\ &= \frac{16kT}{3g_{m1}} \frac{n_f}{4(2R_{ON} + 1/g_{m1})C_1} \\ &= \frac{4kT}{3C_1} \frac{n_f}{(1+x)} \end{aligned} \quad \begin{aligned} \overline{V_{C1,sw2}^2} &= \frac{S_{Ron}(f)}{4\tau} \\ &= \frac{8kTR_{ON}}{4(2R_{ON} + 1/g_{m1})C_1} \\ &= \frac{kT}{C_1} \frac{x}{(1+x)} \end{aligned}$$

Introduced extra parameter $x = 2R_{ON}g_{m1}$

ECE1371

10-22

Noise in a SC Integrator

- Total noise power on C_1 from both phases

$$\begin{aligned} \overline{V_{C1}^2} &= \overline{V_{C1,op}^2} + \overline{V_{C1,sw1}^2} + \overline{V_{C1,sw2}^2} \\ &= \frac{4kT}{3C_1} \frac{n_f}{(1+x)} + \frac{kT}{C_1} \frac{x}{(1+x)} + \frac{kT}{C_1} \\ &= \frac{kT}{C_1} \left(\frac{4n_f/3 + 1 + 2x}{1+x} \right) \end{aligned}$$

Lowest possible noise achieved if $x \rightarrow \infty$

In this case, $\overline{V_{C1}^2} = \frac{2kT}{C_1}$


What was assumed to be the total noise was actually the least possible noise!

ECE1371

10-23

Noise Contributions

- Percentage noise contribution from switches and OTA (assume $n_f=1.5$)

 

ECE1371

10-24

Noise Contributions

- When $g_{m1} \gg 1/R_{ON}$ ($x \gg 1$)...
Switch dominates both bandwidth and noise
Total noise power is minimized
- When $g_{m1} \ll 1/R_{ON}$ ($x \ll 1$)...
OTA dominates both bandwidth and noise
Power-efficient solution
Minimize g_{m1} (and power) for a given settling time and noise

$$g_{m1} = \frac{kT}{\tau V_{C1}^2} \left(\frac{4}{3} n_f + 1 + 2x \right)$$
Minimized for $x=0$

ECE1371

10-25

Maximum Noise

- How much larger can the noise get?
Depends on n_f ... (table excludes cascode noise)


Architecture	Relative V_{EFF} 's	n_f	Maximum Noise ($x=0$)	+dB
Telescopic/ Diff.Pair	$V_{EFF,1}=V_{EFF,n}/2$	1.5	$3kT/C_1$	1.76
Telescopic/ Diff.Pair	$V_{EFF,1}=V_{EFF,n}$	2	$3.67kT/C_1$	2.63
Folded Cascode	$V_{EFF,1}=V_{EFF,n}/2$	2.5	$4.33kT/C_1$	3.36
Folded Cascode	$V_{EFF,1}=V_{EFF,n}$	4	$6.33kT/C_1$	5.01

ECE1371

10-26

Separate Input Capacitors

- Using separate input caps increases noise
Each additional input capacitor adds to the total noise
Separate caps help reduce signal dependent disturbances in the DAC reference voltages

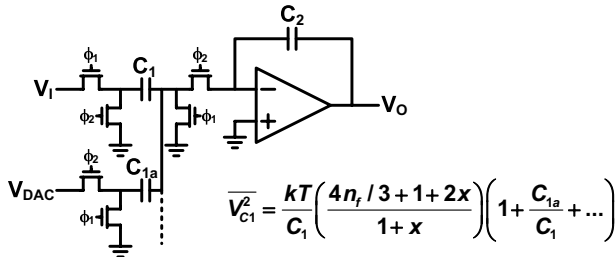

ECE1371

10-27

Differential vs. Single-Ended

- All previous calculations assumed single-ended operation

For same settling time, $g_{m1,2}$ is the same, resulting in the same total power [0dB]

Differential input signal is twice as large [gain 6dB]

Differential operation has twice as many caps and therefore twice as much capacitor noise (assume same size per side – C_1 and C_2) [lose ~1.2dB for $n_f=1.5$, $x=0$... less for larger n_f]

- Net Improvement: ~4.8dB

ECE1371

10-28

Differential vs. Single-Ended

- Single-Ended Noise

$$\overline{V_{C1,se}^2} = \frac{kT}{C_1} \left(\frac{4n_f/3 + 1 + 2x}{1+x} \right)$$

- Differential Noise

$$\begin{aligned} \overline{V_{C1,diff}^2} &= \overline{V_{C1,op}^2} + \overline{V_{C1,sw1}^2} + \overline{V_{C1,sw2}^2} \\ &= \frac{4kT}{3C_1} \frac{n_f}{(1+x)} + \frac{2kT}{C_1} \frac{x}{(1+x)} + \frac{2kT}{C_1} \\ &= \frac{kT}{C_1} \left(\frac{4n_f/3 + 2 + 4x}{1+x} \right) \end{aligned}$$

- Relative Noise (for $n_f=1.5$, $x=0$)

$$\frac{\overline{V_{C1,diff}^2}}{\overline{V_{C1,se}^2}} = \frac{4n_f/3 + 2 + 4x}{4n_f/3 + 1 + 2x} = \frac{4}{3}$$

ECE1371

10-29


Noise in an Integrator

- What is the total output-referred noise in an integrator?

Assume an integrator transfer function

$$H(z) = \frac{kz^{-1}}{1 + \mu(1+k) - (1+\mu)z^{-1}}$$

$$\text{where } k = \frac{C_1}{C_2} \text{ and } \mu = \frac{1}{A}$$

 

ECE1371

10-30

Noise in an Integrator

- Total output-referred noise PSD

$$S_{INT}(f) = S_{C1}(f)|H(z)|^2 + S_{OUT}(f)$$

$$\text{where } \overline{V_{OUT}^2} = \frac{4kT}{3\beta C_O} n_f$$

$$\text{and } \overline{V_{C1}^2} = \frac{kT}{C_1} \left(\frac{4n_f/3 + 1 + 2x}{1+x} \right)$$

Since all noise sources are sampled, white PSDs

$$S_x = \frac{\overline{V_x^2}}{f_s/2}$$

To find output-referred noise for a given OSR

$$\overline{V_{INT}^2} = \int_0^{f_s/(2 \cdot \text{OSR})} S_{INT}(f) df$$

ECE1371

10-31

Noise in a $\Delta\Sigma$ Modulator

- How do we find the total input-referred noise in a $\Delta\Sigma$ modulator?

- 1) Find all thermal noise sources
- 2) Find PSDs of the thermal noise sources
- 3) Find transfer functions from each noise source to the output
- 4) Using the transfer functions, integrate all PSDs from DC to the signal band edge $f_s/2 \cdot \text{OSR}$
- 5) Sum the noise powers to determine the total output thermal noise
- 6) Input noise = output noise (assuming STF is ~ 1 in the signal band)

ECE1371

10-32

Noise in a $\Delta\Sigma$ Modulator

- Example:

$f_s = 100\text{MHz}$, $T = 10\text{ns}$, $\text{OSR} = 32$


$\text{SNR} = 80\text{dB}$ (13-bit resolution)

Input Signal Power = $0.25V^2$ (-6dB from $1V^2$)

Noise Budget: 75% thermal noise

Total input referred thermal noise:

$$\overline{V_{TH}^2} = 0.75 * 10^{(-6 - \text{SNR})/10} = (43.4\mu V)^2$$

 


ECE1371

10-33

Noise in a $\Delta\Sigma$ Modulator

- 1) Find all thermal noise sources

 

$$\overline{V_{ni1}^2} = \frac{kT}{C_{1A}} \left(\frac{4n_{fA}/3 + 1 + 2x_A}{1+x_A} \right) \quad \overline{V_{ni2}^2} = \frac{kT}{C_{1B}} \left(\frac{4n_{fB}/3 + 1 + 2x_B}{1+x_B} \right)$$

$$\overline{V_{no1}^2} = \frac{4kT}{3\beta_A C_{OA}} n_{fA} \quad \overline{V_{no2}^2} = \frac{4kT}{3\beta_B C_{OB}} n_{fB}$$

$$\overline{V_{n3}^2} = \frac{2kT}{C_{f1}} \left(1 + \frac{C_{f2}}{C_{f1}} + \frac{C_{f3}}{C_{f1}} \right) = \frac{2kT}{C_{f1}} (1 + 2 + 1)$$

ECE1371

10-34

Noise in a $\Delta\Sigma$ Modulator

- 2) Find PSDs of the thermal noise sources

For each of the mean square voltage sources,

$$S_x = \frac{\overline{V_x^2}}{f_s/2}$$

- 3) Find transfer functions from each noise source to the output

Assume ideal integrators

$$H_A(z) = H_B(z) = \frac{z^{-1}}{1-z^{-1}}$$

$$\text{STF}(z) = 1$$

$$\text{NTF}(z) = (1-z^{-1})^2 = \frac{1}{1+2H(z)+H(z)^2}$$

ECE1371

10-35

Noise in a $\Delta\Sigma$ Modulator

- 3) Find transfer functions from each noise source to the output

From input of $H_A(z)$ to output...

$$\begin{aligned} \text{NTF}_{i1}(z) &= (2H(z) + H(z)^2) \text{NTF}(z) \\ &= \frac{2H(z) + H(z)^2}{1+2H(z)+H(z)^2} = 2z^{-1} - z^{-2} \end{aligned}$$

From output of $H_A(z)$ to output...

$$\begin{aligned} \text{NTF}_{o1}(z) &= (2 + H(z)) \text{NTF}(z) \\ &= \frac{2 + H(z)}{1+2H(z)+H(z)^2} = (1-z^{-1})(2-z^{-1}) \end{aligned}$$

ECE1371

10-36

Noise in a $\Delta\Sigma$ Modulator

- 3) Find transfer functions from each noise source to the output to the output

From input of $H_B(z)$ to output...

$$\begin{aligned} NTF_{i2}(z) &= H(z)NTF(z) \\ &= \frac{H(z)}{1 + 2H(z) + H(z)^2} = z^{-1}(1 - z^{-1}) \end{aligned}$$

From output of $H_B(z)$ to output (equal to transfer function at input of summer to output)...

$$NTF_{o2}(z) = NTF(z) = (1 - z^{-1})^2$$


ECE1371

10-37

Noise in a $\Delta\Sigma$ Modulator

- 3) Find transfer functions from each noise source to the output to the output

Most significant is NTF_{i1}

 

ECE1371

10-38

Noise in a $\Delta\Sigma$ Modulator

- 4) Using the transfer functions, integrate all PSDs from DC to the signal band edge $f_s/2 \cdot OSR$

Use MATLAB/Maple to solve the integrals...

$$\begin{aligned} \overline{N_{i1}^2} &= \frac{\overline{V_{ni1}^2}}{f_s/2} \int_0^{f_s/(2 \cdot OSR)} |NTF_{i1}(f)|^2 df \\ &= \frac{\overline{V_{ni1}^2}}{f_s/2} \left[\frac{5f_s}{2 \cdot OSR} - \frac{2f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \right] \\ \overline{N_{o1}^2} &= \frac{\overline{V_{no1}^2}}{f_s/2} \int_0^{f_s/(2 \cdot OSR)} |NTF_{o1}(f)|^2 df \\ &= \frac{\overline{V_{no1}^2}}{f_s/2} \left[\frac{7f_s}{OSR} + \frac{2f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \cos\left(\frac{\pi}{OSR}\right) - \frac{9f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \right] \end{aligned}$$

ECE1371

10-39

Noise in a $\Delta\Sigma$ Modulator

- 4) Using the transfer functions, integrate all PSDs from DC to the signal band edge $f_s/2 \cdot OSR$

$$\begin{aligned} \overline{N_{i2}^2} &= \frac{\overline{V_{ni2}^2}}{f_s/2} \left[\frac{f_s}{OSR} - \frac{f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \right] \\ \overline{N_{o2}^2} &= \frac{\overline{V_{no2}^2} + \overline{V_{n3}^2}}{f_s/2} \left[\frac{3f_s}{OSR} + \frac{f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \cos\left(\frac{\pi}{OSR}\right) - \frac{4f_s}{\pi} \sin\left(\frac{\pi}{OSR}\right) \right] \end{aligned}$$

(Some simplifications can be made for large OSR)

ECE1371

10-40

Noise in a $\Delta\Sigma$ Modulator

- 5) Sum the noise powers to determine the total output thermal noise

Assume $x_A = x_B = 0.1$ and $n_{fA} = n_{fB} = 1.5$

$$\begin{aligned} \overline{V_{TH}^2} \approx & \frac{2.9kT}{C_{1A}} \frac{1}{OSR} + \frac{2kT}{\beta_A C_{OA}} \frac{\pi^2}{3OSR^3} + \frac{2.9kT}{C_{1B}} \frac{\pi^2}{3OSR^3} \\ & + \frac{2kT}{\beta_B C_{OB}} \frac{\pi^4}{5OSR^5} + \frac{8kT}{C_{f1}} \frac{\pi^4}{5OSR^5} \end{aligned}$$

With an OSR of 32, first term is most significant (assume $\beta_A = \beta_B = 1/3$)

$$\overline{V_{TH}^2} \approx 9.1 \times 10^{-2} \frac{kT}{C_{1A}} + 6.0 \times 10^{-4} \frac{kT}{C_{OA}} + 2.9 \times 10^{-4} \frac{kT}{C_{1B}} + \dots$$

ECE1371

10-41

Noise in a $\Delta\Sigma$ Modulator

- 6) Input noise = output noise (assuming STF is ~ 1 in the signal band)

$$\begin{aligned} \overline{V_{TH}^2} &\approx 9.1 \times 10^{-2} \frac{kT}{C_{1A}} = (43.4 \mu V)^2 \\ \Rightarrow C_{1A} &= 200 \text{ fF} \end{aligned}$$

Assuming other capacitors are smaller than C_{1A} , then subsequent terms are insignificant and the approximation is valid

If lower oversampling ratios are used, other terms may become more significant in the calculation

ECE1371

10-42

Noise in a Pipeline ADC

- Similar procedure to $\Delta\Sigma$ modulator, except transfer functions are much easier to compute

- Differences...

Input refer all noise sources

Gain from each stage to the input is a scalar

Noise from later stages will be more significant since typical stage gains are as low as 2

Sample-and-Hold adds extra noise which is input referred with a gain of 1

Entire noise power is added since the signal band is from 0 to $f_s/2$ (OSR=1)

ECE1371

10-43


Noise in a Pipeline ADC

- Example

If each stage has a gain G_1, G_2, \dots, G_N

$$\overline{N_i^2} = \overline{V_{ni1}^2} + \frac{\overline{V_{no1}^2} + \overline{V_{ni2}^2}}{G_1^2} + \frac{\overline{V_{no2}^2} + \overline{V_{ni3}^2}}{G_1^2 G_2^2} + \dots + \frac{\overline{V_{noN}^2}}{G_1^2 G_2^2 \dots G_N^2}$$

S/H stage noise will add directly to V_{ni1}

 

ECE1371

10-44

NLCOTD: Gain Booster CMFB

What You Learned Today

1. Noise analysis for switched-capacitor circuits
2. Contributions of both switch noise and OTA noise
 - Finding a power efficient solution
 - Significance of OTA architecture
3. $\Delta\Sigma$ modulator design example

ECE1371

10-45

ECE1371

10-46

Some Project Guidelines

- General:
 - 1) Corners: Do not need to simulate
 - 2) Noise analysis: use calculations to size the capacitors, but use Cadence to find OTA noise
 - 3) Clock Generator: don't need to design non-overlapping clock generator, but buffer the ideal clocks and take into account the buffer size for power calculations (if you have other clock phases – not just ϕ_1 and ϕ_2 – you should indicate how you would generate these)
 - 4) Biasing: Ideal voltage source for VDD/VSS and reference ladder edges; Ideally one current source from which all currents are derived (at least use only one current source per circuit block)

ECE1371

10-47

Some Project Guidelines

- Presentation: 15-20 minutes
 - 12 Slides (1 title, 11 content)
 - Focus on major design issues and circuit blocks (what you consider the most important design decisions)
- Report
 - We should be able to replicate your circuit with the information provided in the report
 - Give transistor sizes, preferably annotated on figures
 - Try to avoid Cadence schematics (if you use them, make them more readable without all the unnecessary annotations)

ECE1371

10-48